

ECE 5610 Lab 4

Boost Converter

Objective

The objective of this experiment is to study the characteristics of a simple boost converter. The circuit will be operated under continuous conduction mode (CCM) and open loop conditions (no feedback). Our main goal will be to compare the theoretical results with the experimental results.

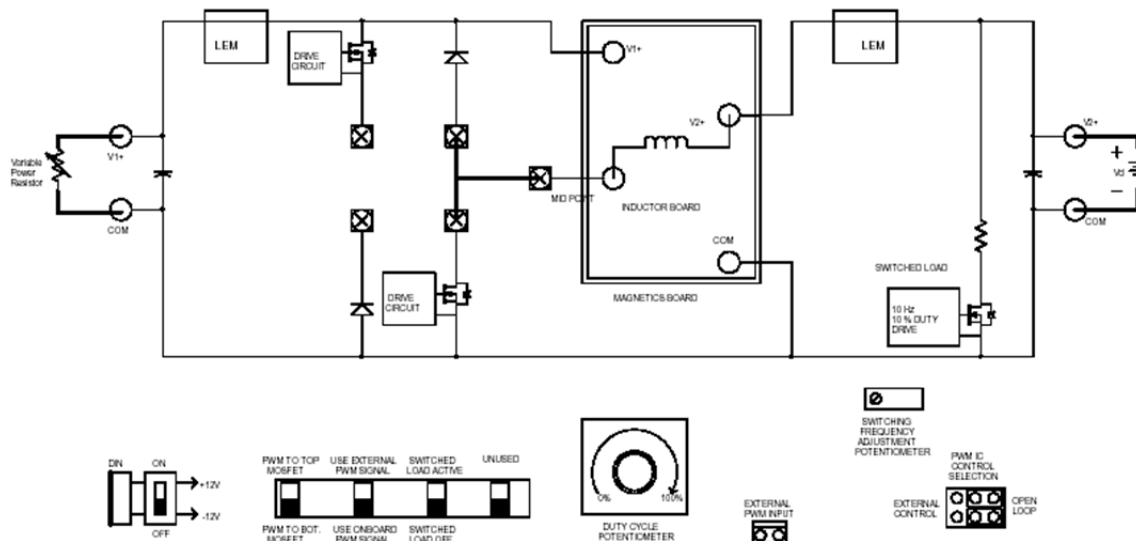


Figure 3.1: Schematic of Boost Converter

Note 1: The oscilloscope channels share the same signal GND. Therefore, it is recommended to take precautions while measuring two quantities having separate reference potentials. Students are advised to use the circuit connections shown in Figure 3 of Lab 1 if you need to take two measurements simultaneously in the oscilloscope.

Note2: Care must be taken while conducting the boost converter experiment. Students need to make sure that the load is always connected at the output of the constructed boost converter.

4.1 Preparing the setup

Make the connections on the power-pole board as shown in Fig. 3.1.

- Use the magnetic board BB board for the boost converter circuit. The inductor is $100 \mu\text{H}$.
- Use a variable load resistor (R_L) as a load.
- Use onboard PWM signals.
- Connect the ± 12 signal supply at the DIN connector. Signal supply switch S90 should be in OFF position.

4.2 Checks before powering the circuit

- Check the circuit connections as per the schematic.
- Have your circuit checked by your **Lab TA**.

4.3 Powering the circuit

- Switch ON the signal supply. The green LED should illuminate.
- Adjust the duty ratio to 10%.
- Set the load resistance $R_L = 20 \Omega$.
- Adjust the switching frequency to 100 kHz.

→ Power supply @
0.56A / 9.8V

10/16/2021

- Apply input voltage V_d of 10 V at terminals V2+ and COM.

— 10.1 V

4.4 Measurement and waveforms

Take the following measurements,

4.4.1 Varying the duty ratio

- Set the duty ratio to 10%, switching frequency at 100 kHz and $R_L = 20 \Omega$.
- Vary the duty ratio from 10% to 60% (in steps of 10%).
- Measure the average output voltage for the corresponding duty ratios.
- Calculate the theoretical average output voltage for the corresponding duty ratios.

starting @ scope 50 mV

4.4.2 Varying the switching frequency

- Set the duty ratio to 50%, switching frequency at 100 kHz and $R_L = 20 \Omega$.
- Measure the peak-peak input current ripple.
- Observe and make a copy of the input current (CS5) waveform.
- Repeat the above procedure for different switching frequencies (40 kHz, 60 kHz, and 80 kHz).

4.4.3 Determining the efficiency

- Set duty ratio at 50%.
- Set load resistance $R_L = 20 \Omega$.
- Measure the RMS output current I_o .
- Measure the RMS input current I_i .
- Measure the RMS output voltage.
- Measure the RMS input voltage.
- Calculate the efficiency of the boost converter for different frequencies (60 kHz and 100 kHz) using the above measurements.

4.5 Lab report

The lab report should have a brief abstract detailing what has been done in this experiment. The remaining part of the report should consist of the information asked below along with any discussion you feel necessary.

1. Attach a graph output voltage (V1+) versus duty ratio using data obtained in section 4.4.1. Also plot the theoretically calculated results on the same graph. Compare these two plots and comment about how the boost converter works as a variable dc step up transformer. Enclose output voltage waveform for duty ratio 50%.
2. Attach a copy of the input/inductor current (CS5) waveform obtained in section 4.4.2.
3. Plot the peak-peak ripple in the input current versus switching frequency using data obtained in section 4.4.2. Plot the theoretical results on the same graph. Compare these two plots.
4. Comment on the difference in efficiency results obtained for two switching frequencies.

4.4.1 | Use pin #50 outputs @ 100kHz

Duty	10%	20%	30%	40%	50%	60%
V_o	10.3	11.58	13.2	15.3	18.2	21.3
PSU						
A	0.54	0.73	0.95	1.23	1.43	2.59 A
V	10V	10V	10V	10V	10V	10V

4.4.2 |

50% @ 100kHz \rightarrow 440mV

Scope SS ch 2 @ input (PSU)

@ 40kHz \rightarrow 400mV

@ 60kHz \rightarrow 430mV

@ 40kHz \rightarrow 450mV

4.4.3

$$R_L = 20 \Omega$$

$$V_o = 17.2V$$

$$I_o = 0.91A$$

$$V = IR$$

$$I = \frac{V}{R} = \frac{17.2}{20} = 0.91A$$

$$V_{in} = 10V$$

$$I_{in} = 1.73$$

50% @ 100 kHz

$$\eta = \frac{P_o}{P_{in}} = \frac{16.562}{17.3} = 0.9050 \approx 90.5\%$$

$$V_o = 17.2V$$

$$I_o = 0.91A$$

$$R_L = 20 \Omega$$

$$I_o = \frac{V}{R} = \frac{17.2}{20} = 0.91A$$

50% @ 60 kHz

$$V_{in} = 10V$$


$$I_{in} = 1.74A$$

$$I_{in_ripple} = 430mV$$

$$\hookrightarrow \eta = \frac{P_o}{P_{in}} = \frac{17.2(0.91)}{10V(1.74)} = 0.9001 \approx 90.01\%$$

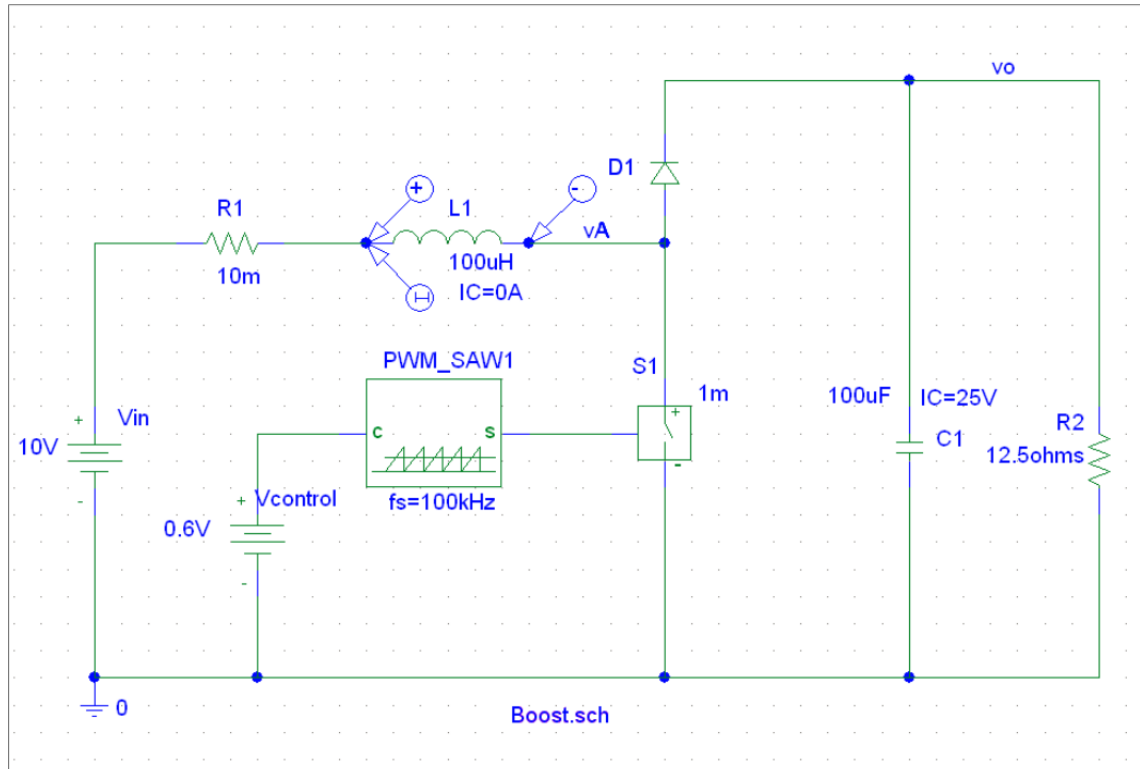4.6 Spice simulation of the Boost converter

We will use this simulation to observe switching waveforms in a near-ideal boost converter operating at a fixed duty cycle. Open the file **Boost.sch**. Take a moment to examine the circuit, and then perform the following measurements.



Assignments:

1. Plot the waveforms during the last 10 switching cycles for i_L , v_L and v_o . You need to make sure the circuit has reached steady state. Depending on the operating conditions, you may need to simulate the circuit for a much longer time (way more than 10 switching cycles).
2. Plot the average value of v_L .
3. Plot i_L and measure the peak-peak ripple Δi_L and compare it with the equation in the text book.
4. Plot i_{diode} and i_C waveforms. What is the average value of i_C ? Compare this i_C waveform with the ripple in i_{diode} .
5. Plot the input current waveform and calculate its average. Compare that to the value obtained from the theoretical calculations.
6. Calculate the inductance value of L , if $\Delta i_L = 1/3^{\text{rd}}$ of the input current. Verify these computed results with the results obtained from the simulation.
7. Change the output power in this circuit to one-half its original value. Measure the peak-peak ripple Δi_L and compare it with that in assignment 3. Comment on this comparison.
8. Calculate R_{crit} and verify whether the converter is operating on the boundary of CCM and DCM.